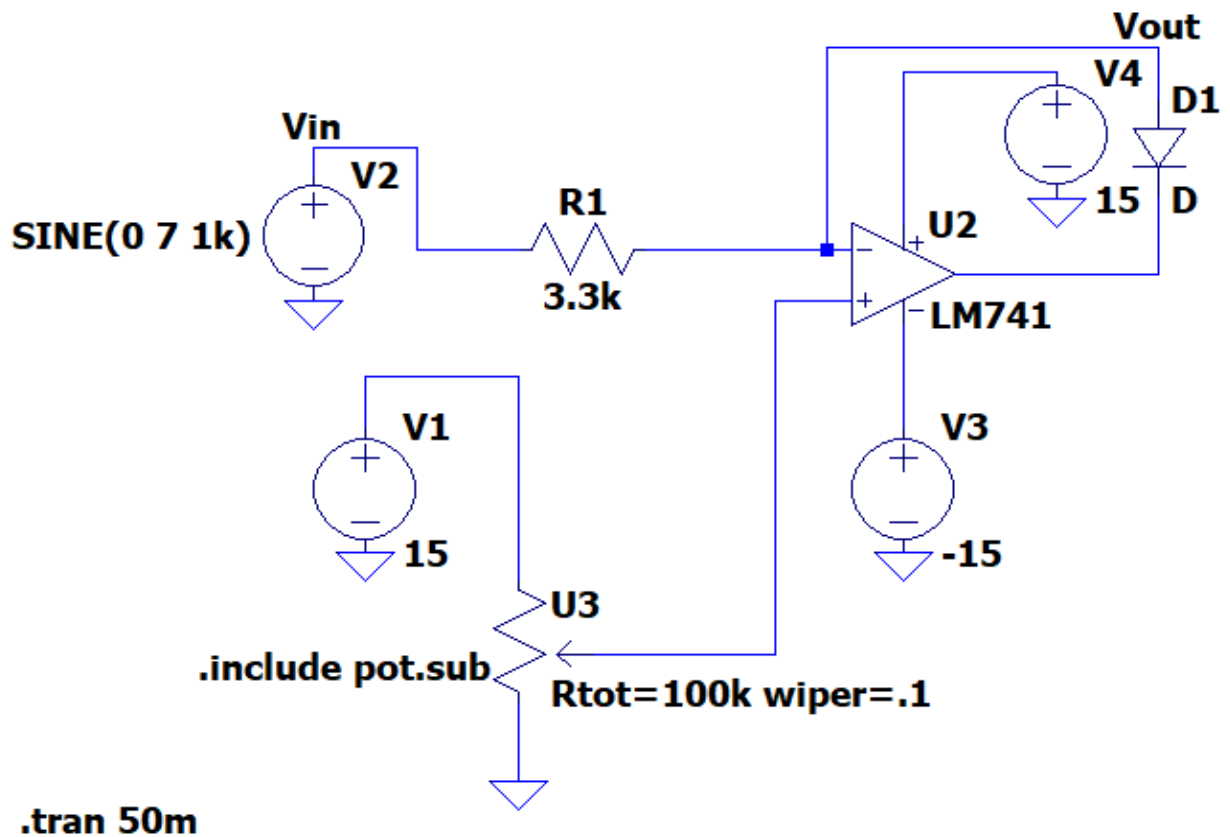


# VARIABLE CLIPPER CIRCUIT

Circuit diagram:



The clipping voltage can be varied by moving the wiper in the potentiometer.

Simulation:

